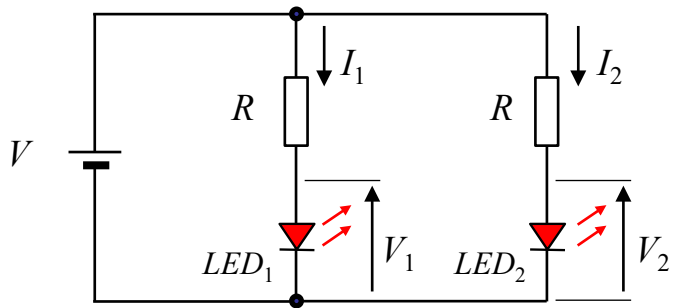


デジタル回路講義資料

第5回 NAND, NOR, XOR回路

担当：古橋武




$$I_1 = \frac{V - V_1}{R}$$

$$I_2 = \frac{V - V_2}{R}$$

$V = 3[\text{V}], V_1 = V_2 = 1.8[\text{V}], R = 500[\Omega]$ とすると

$$I_1 = I_2 = \frac{3 - 1.8}{500} = 2.4 [\text{mA}]$$

LED_1, LED_2 は明るく点く

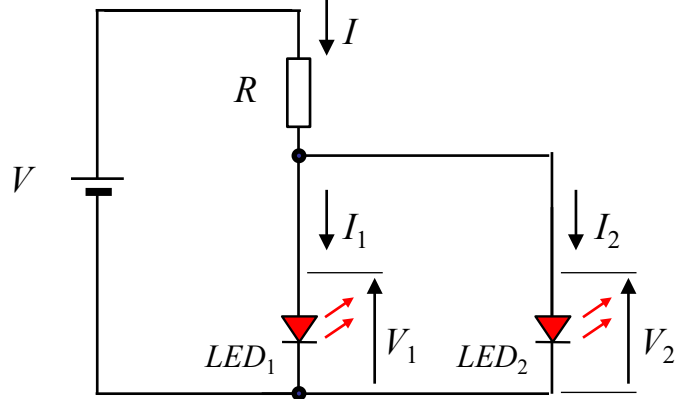

$$I = \frac{V - V_s}{R} \quad (V_s \text{ は } V_1, V_2 \text{ のうち低い方})$$


$V = 3[\text{V}], V_1 = V_2 = 1.8[\text{V}], R = 500[\Omega]$ とすると

$$I = \frac{3 - 1.8}{500} = 2.4 [\text{mA}]$$

$$I_1 = I_2 = \frac{I}{2} = 1.2 [\text{mA}]$$



LED_1, LED_2 は暗く点く.

LEDの特性


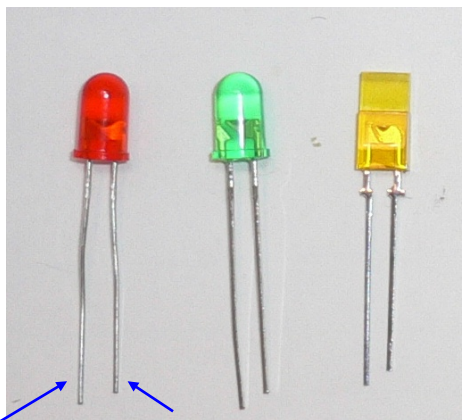


アノード
[足の長い方]

カソード

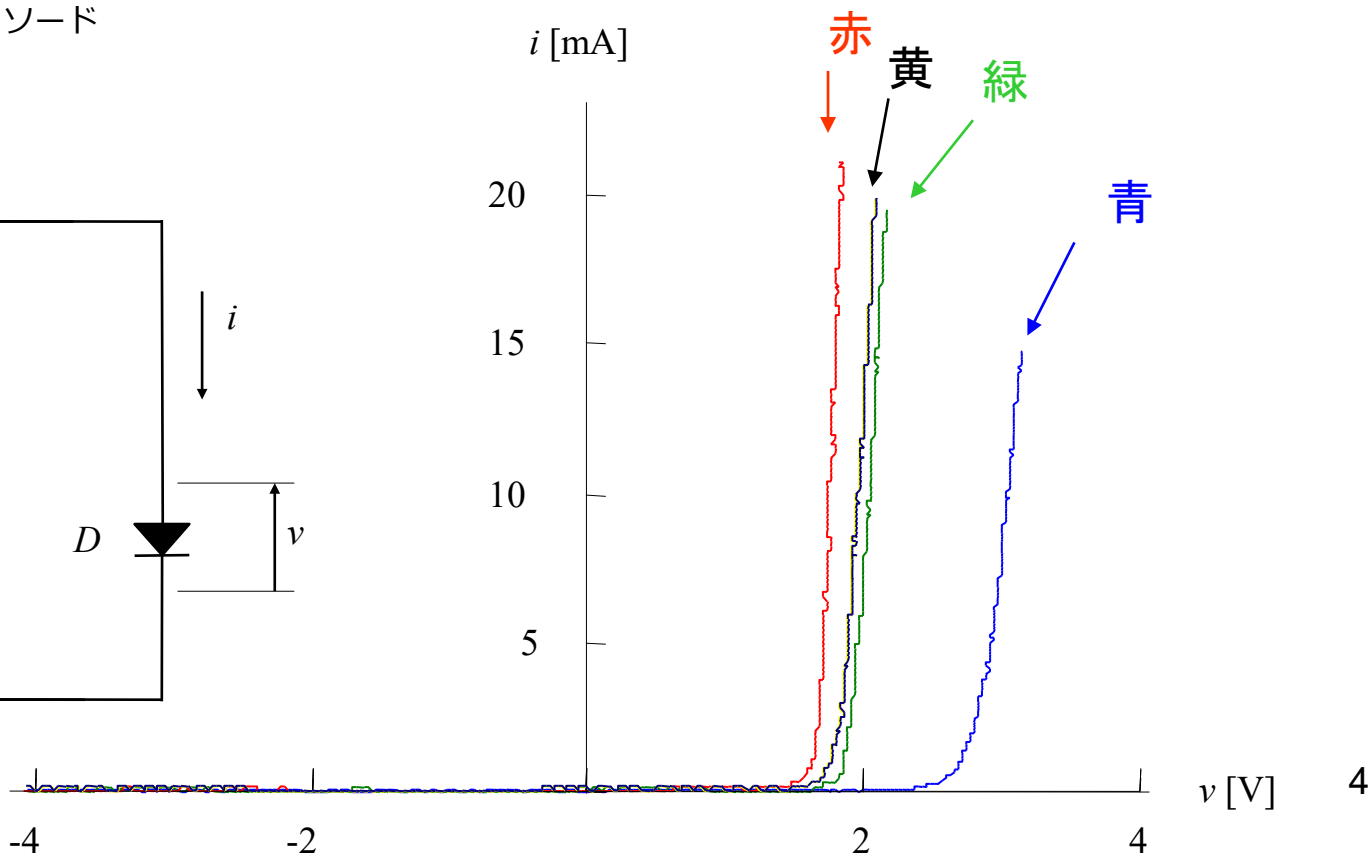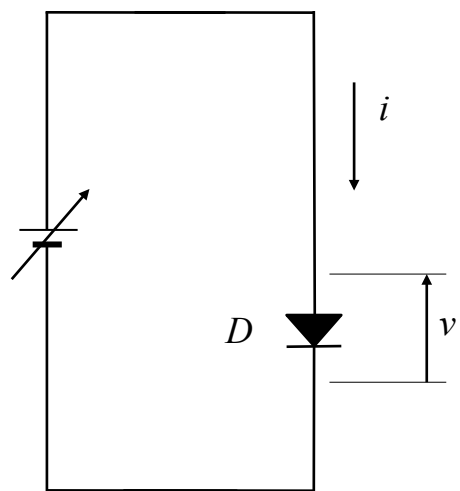



赤だけ点いて，緑は点かない。

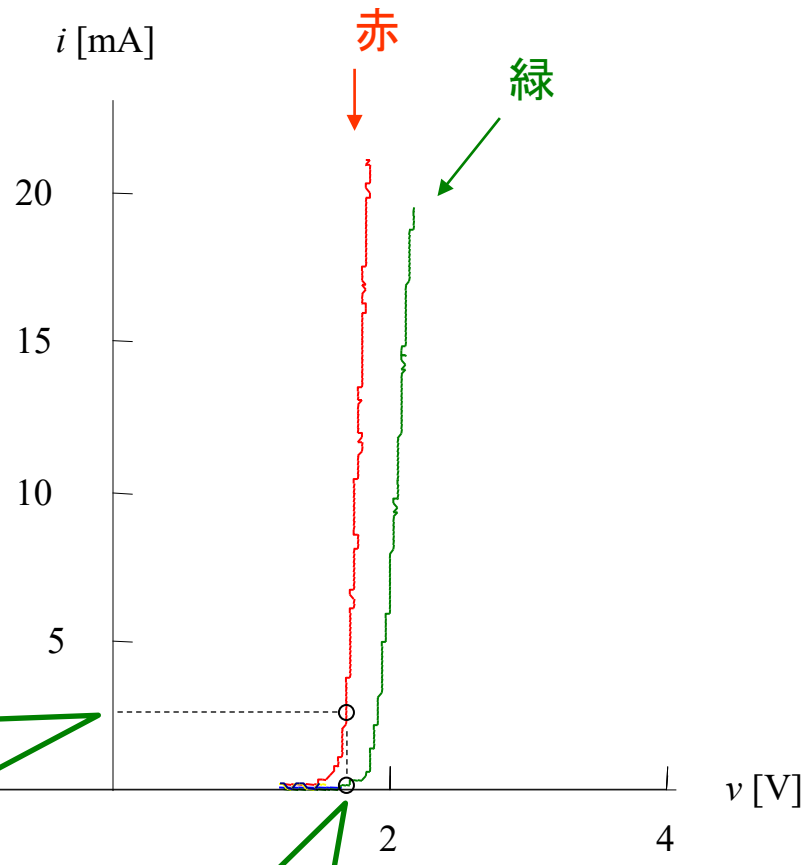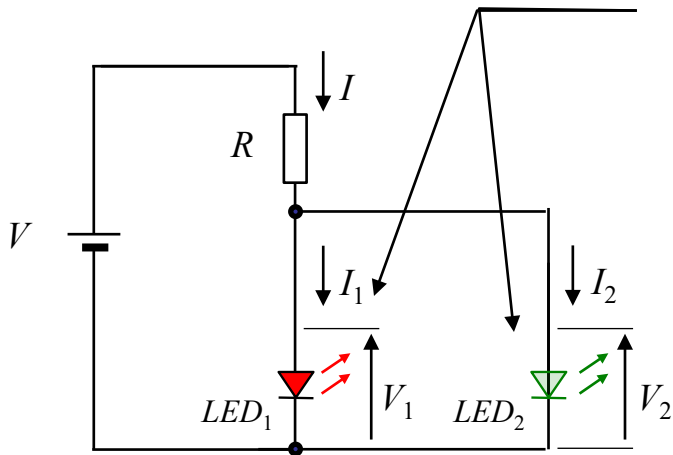


$I_1 = 2.4$ [mA]
 $I_2 = 0$ [mA]

$V_1 = V_2$

NAND回路

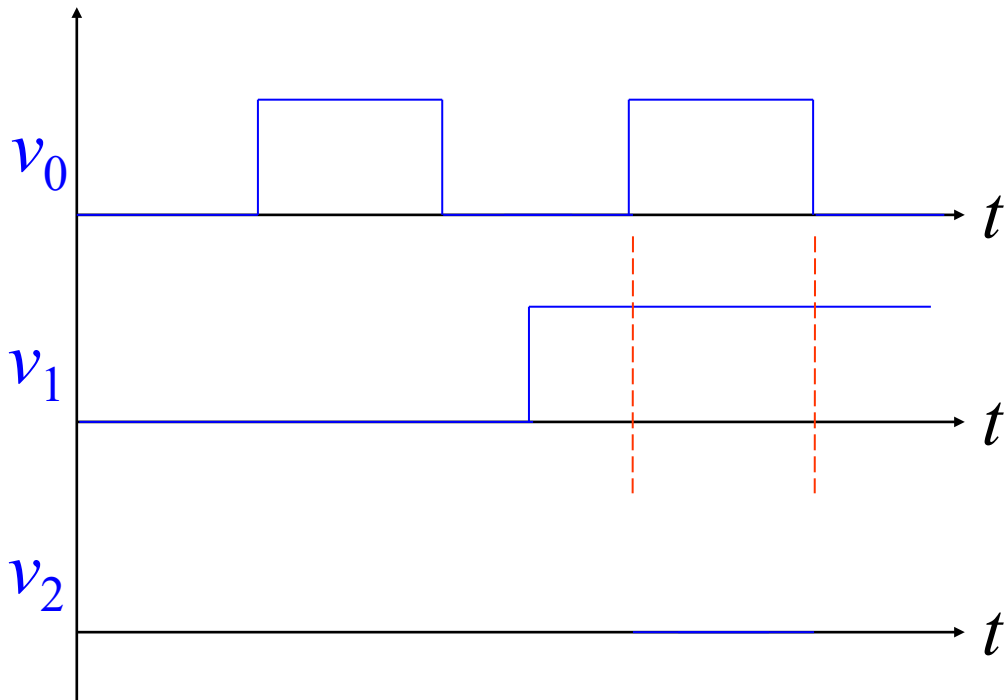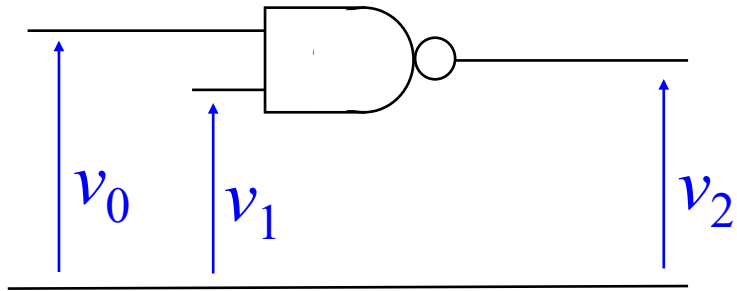


4.5V =

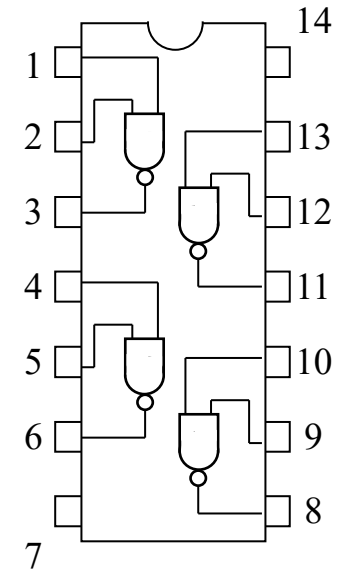


TC74HC00AP
NAND回路

NAND回路


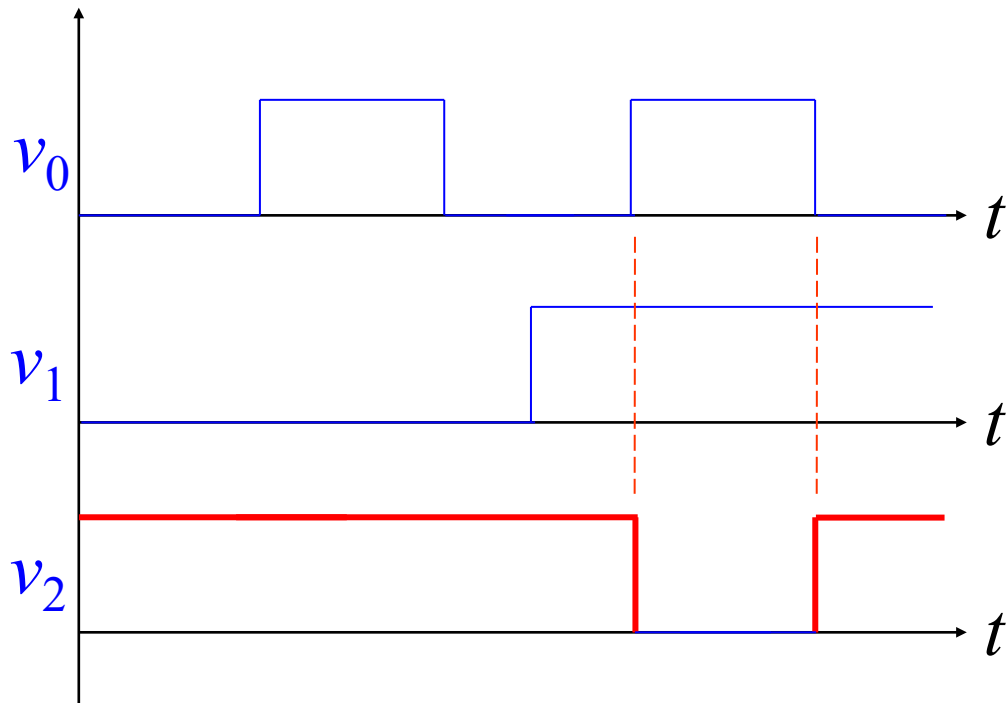


タイムチャート

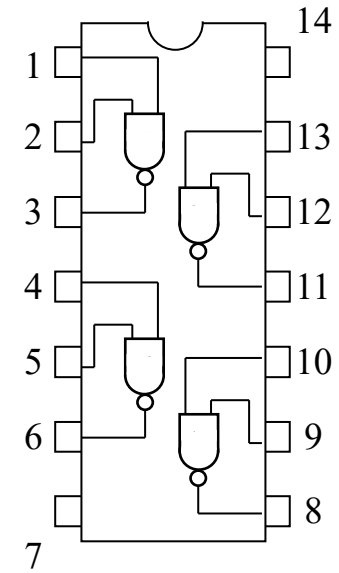


TC74HC00AP
NAND回路


NAND回路

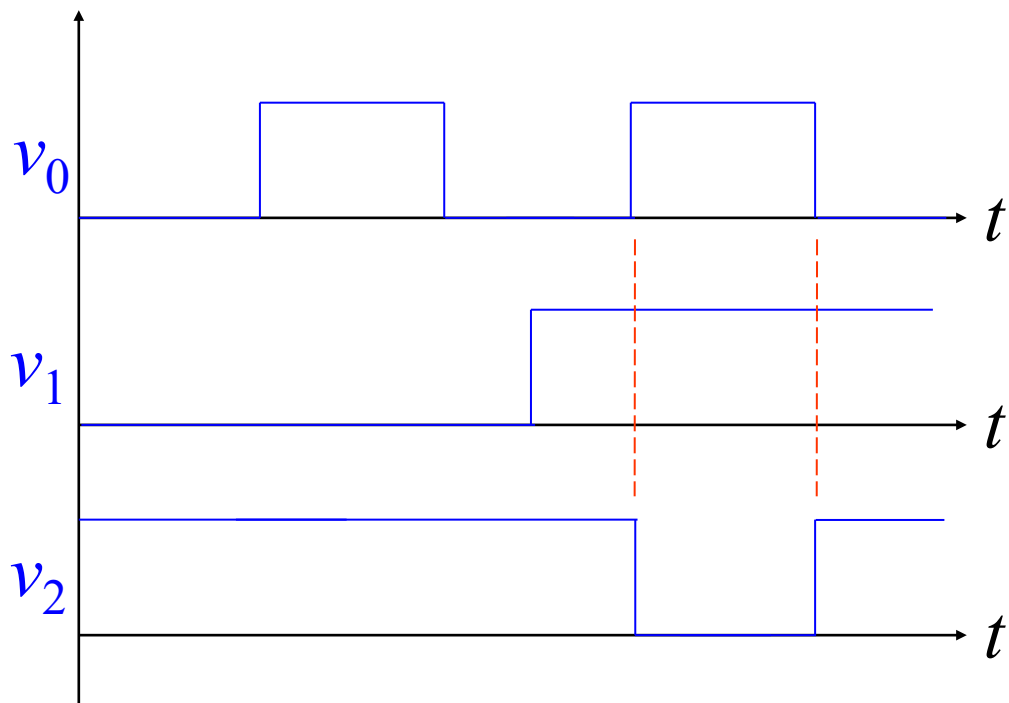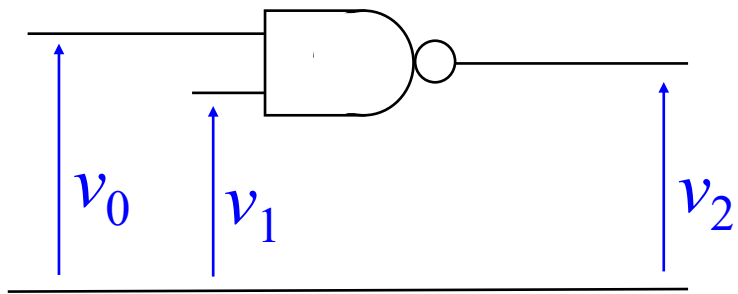

タイムチャート

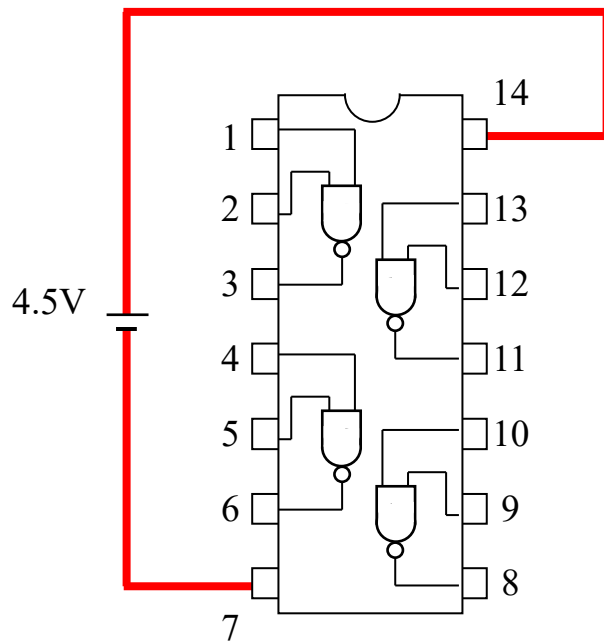


TC74HC00AP
NAND回路

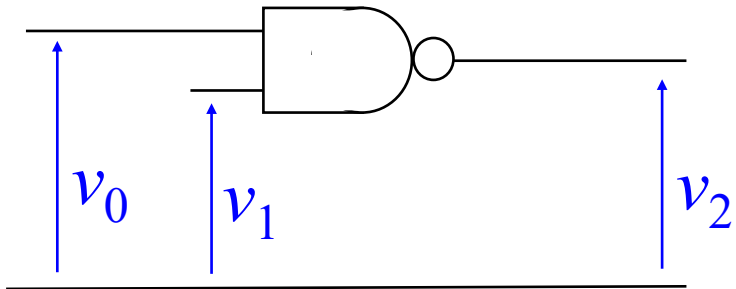


v_1 [V]	v_0 [V]	v_2 [V]
-----------	-----------	-----------

真理值表

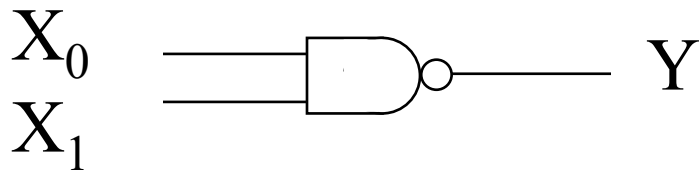


$Y =$

X_1	X_0	Y
-------	-------	-----

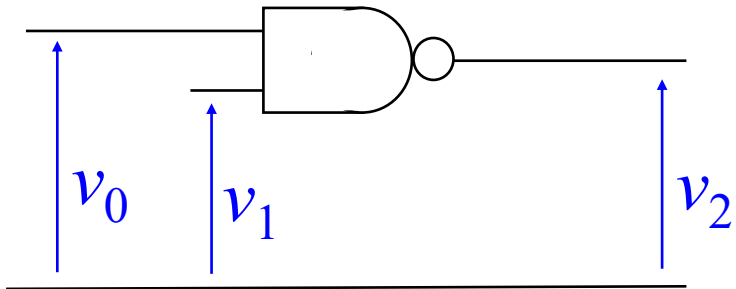


v_1 [V]	v_0 [V]	v_2 [V]
0	0	4.5
0	4.5	4.5
4.5	0	4.5
4.5	4.5	0

真理值表

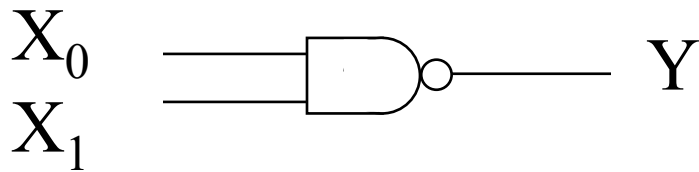


$Y =$

X_1	X_0	Y

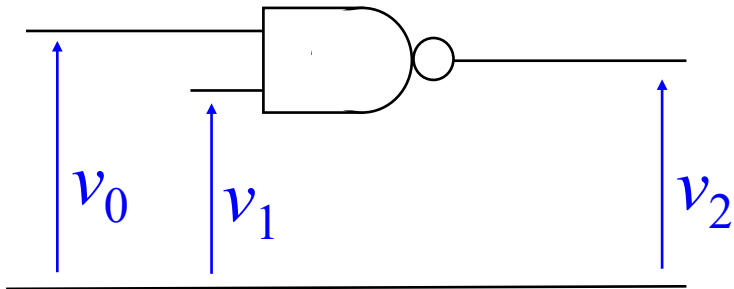

v_1 [V]	v_0 [V]	v_2 [V]
0	0	4.5
0	4.5	4.5
4.5	0	4.5



真理值表

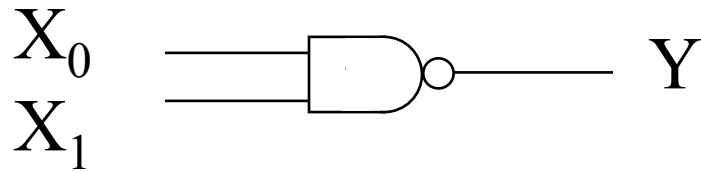


$$Y = \overline{X_1 X_0}$$

X_1	X_0	Y
0	0	1
0	1	1
1	0	1
1	1	0

NOR回路

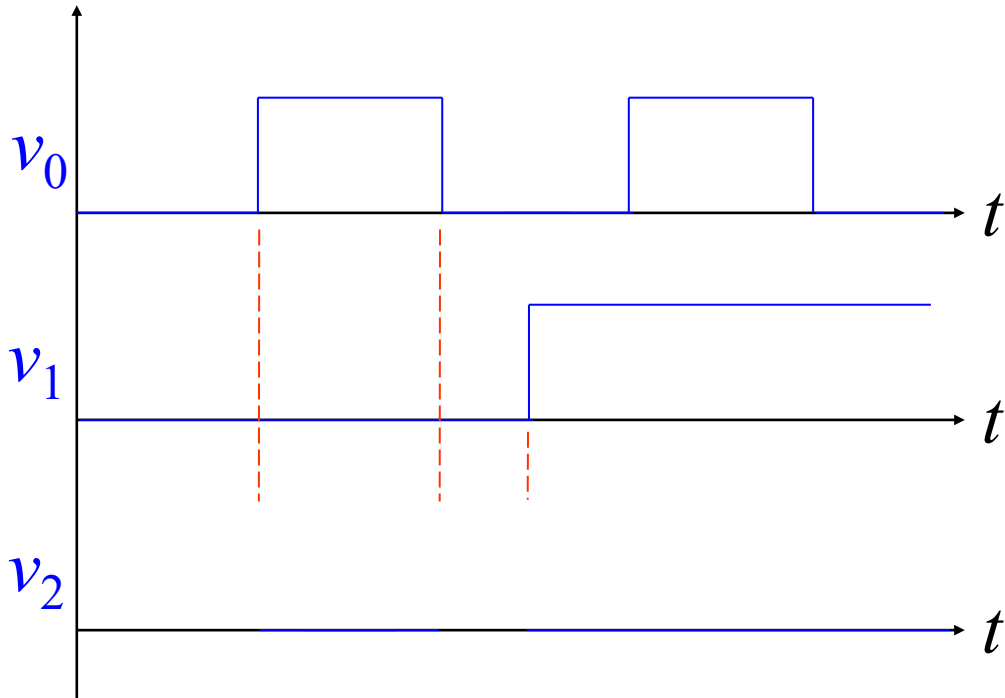
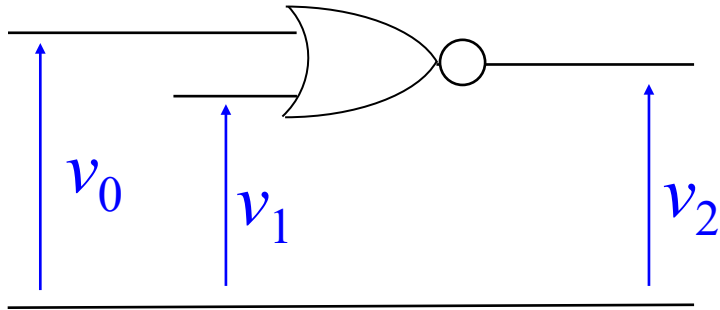


タイムチャート

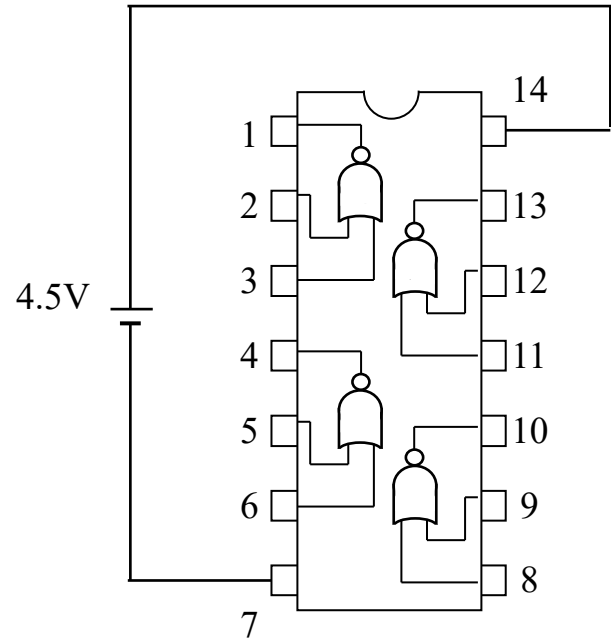


TC74HC02AP
NOR回路

NOR回路

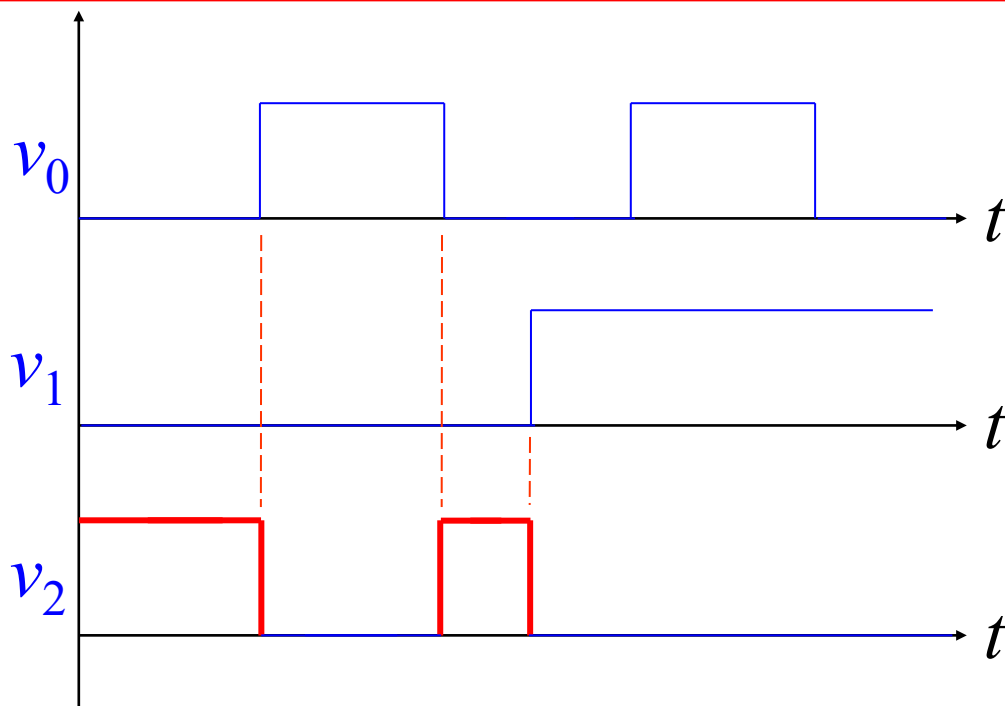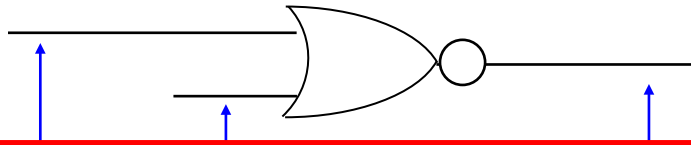


タイムチャート

4.5V

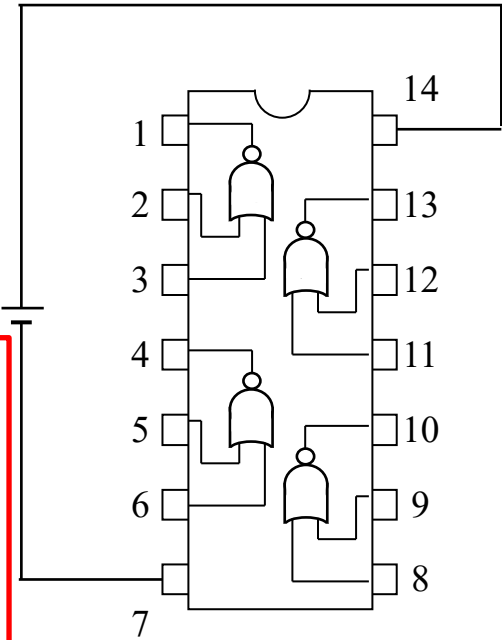


TC74HC02AP
NOR回路

$v_1[V]$	$v_0[V]$	$v_2[V]$
----------	----------	----------

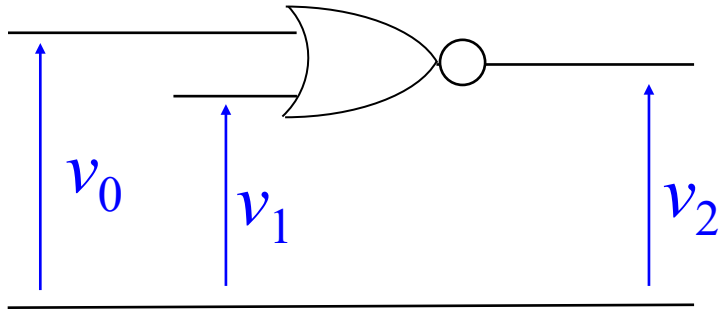


真理值表

X_1	X_0	Y
-------	-------	-----

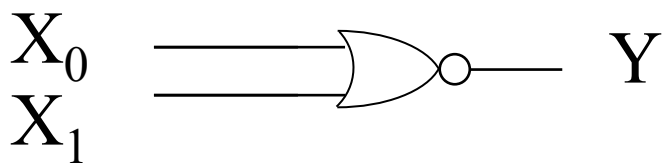


$Y =$

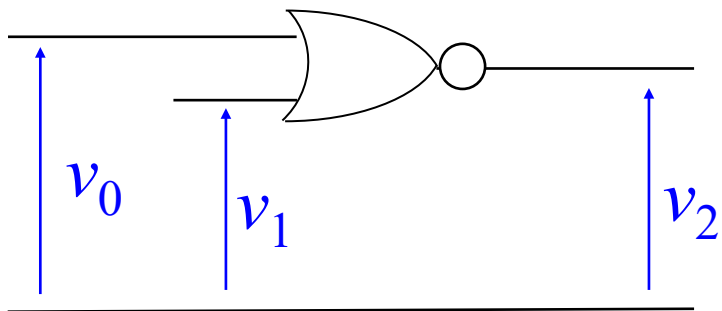


v_1 [V]	v_0 [V]	v_2 [V]
0	0	4.5
0	4.5	0
4.5	0	0
4.5	4.5	0

真理值表

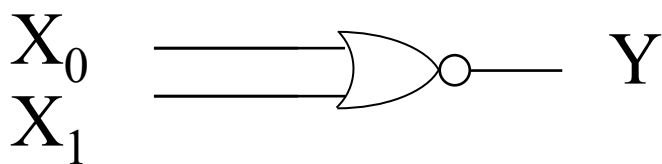


$Y =$

X_1	X_0	Y
-------	-------	-----

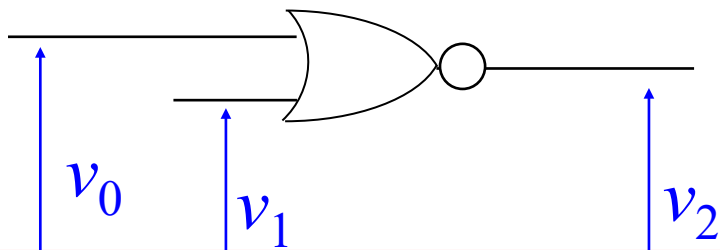

v_1 [V]	v_0 [V]	v_2 [V]
0	0	4.5
0	4.5	0
4.5	0	0



真理值表

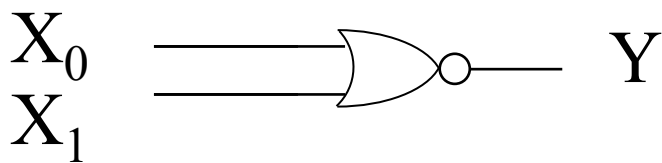


$$Y = \overline{X_1 + X_0}$$

X_1	X_0	Y
0	0	1
0	1	0
1	0	0
1	1	0

XOR回路

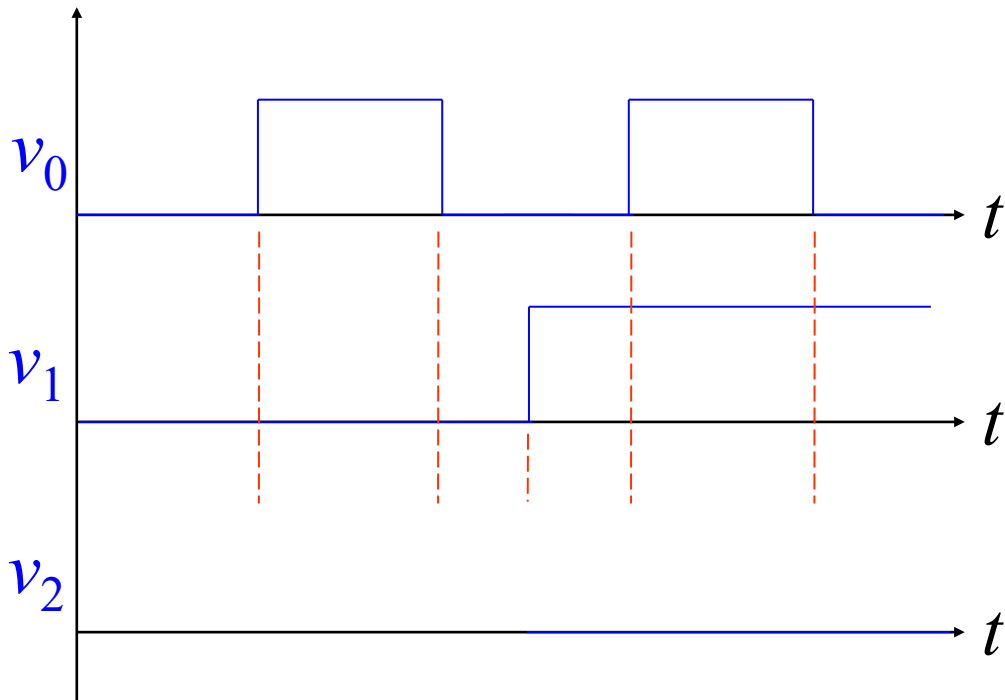
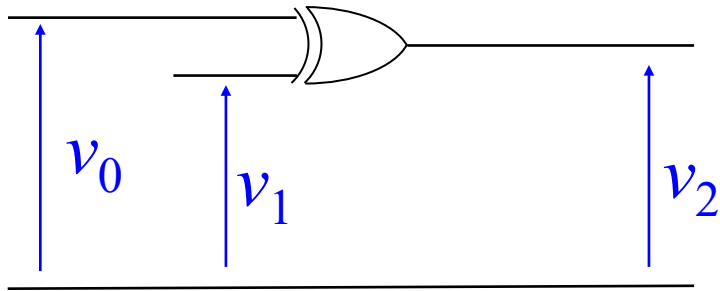


タイムチャート

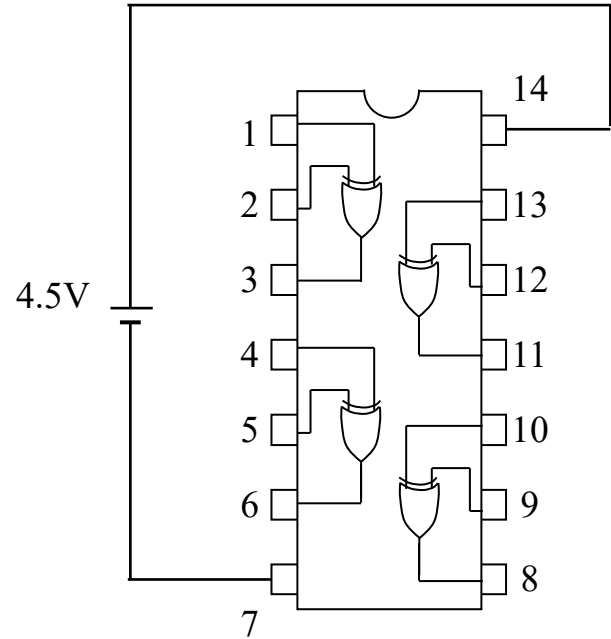


TC74HC86AP
XOR回路

XOR回路

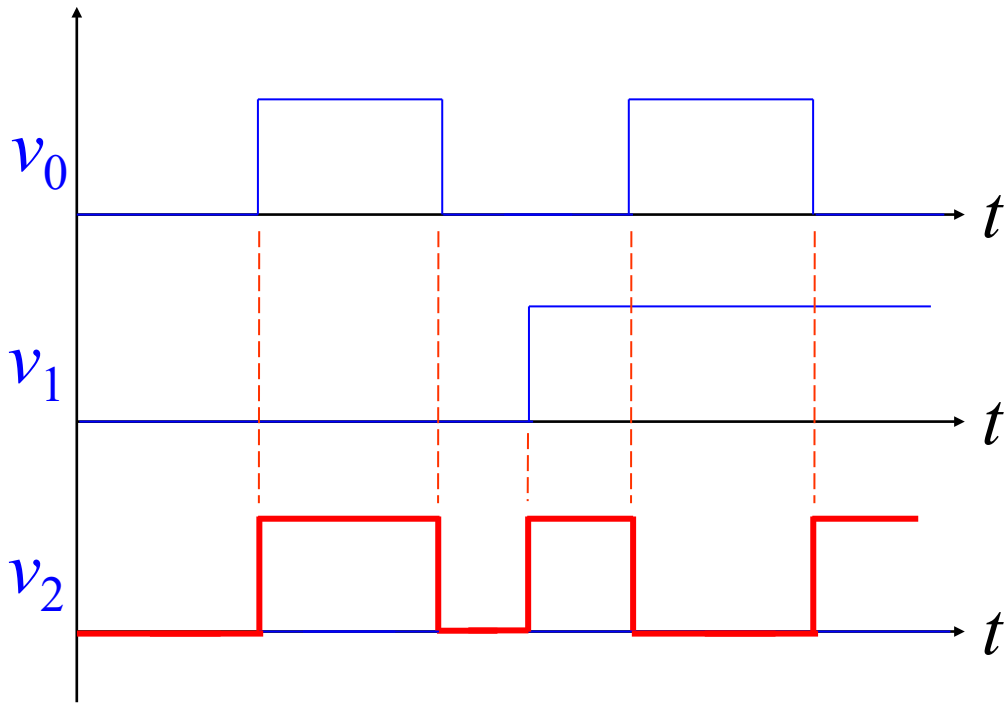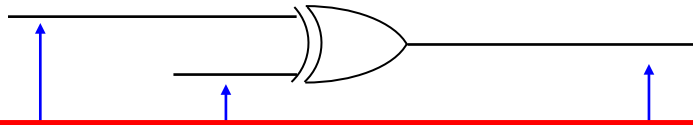


タイムチャート

4.5V

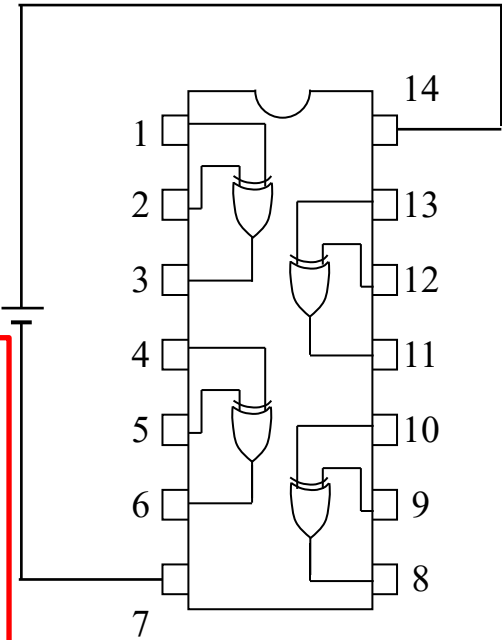


TC74HC86AP
XOR回路

$v_1[V]$	$v_0[V]$	$v_2[V]$
----------	----------	----------

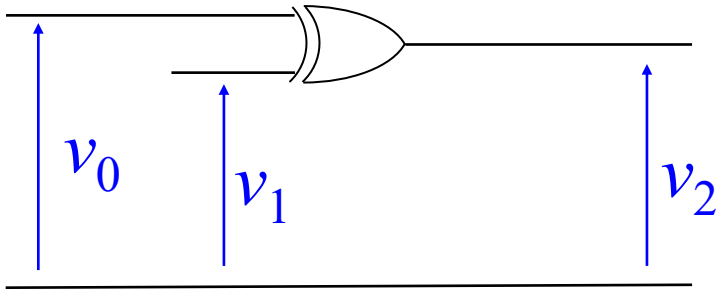


真理值表

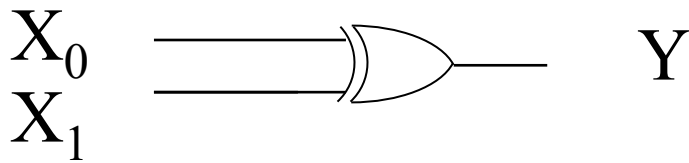


X_1	X_0	Y
-------	-------	-----

$Y =$

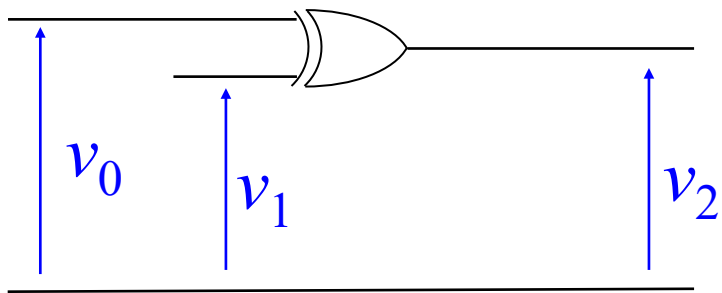



v_1 [V]	v_0 [V]	v_2 [V]
0	0	0
0	4.5	4.5
4.5	0	4.5
4.5	4.5	0

真理值表

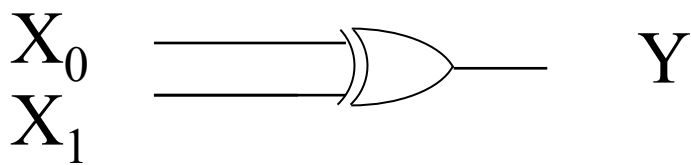

$Y =$

X_1	X_0	Y
-------	-------	-----

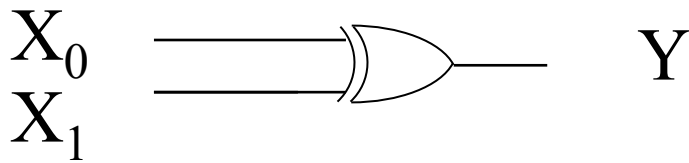
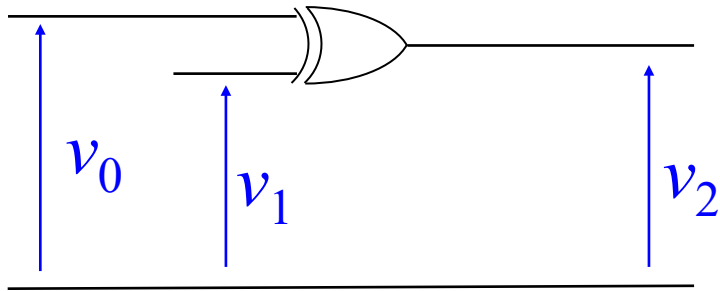


$Y =$

v_1 [V]	v_0 [V]	v_2 [V]
0	0	0
0	4.5	4.5

真理值表

X_1	X_0	Y
0	0	0
0	1	1
1	0	1
1	1	0

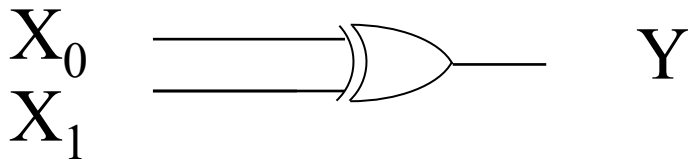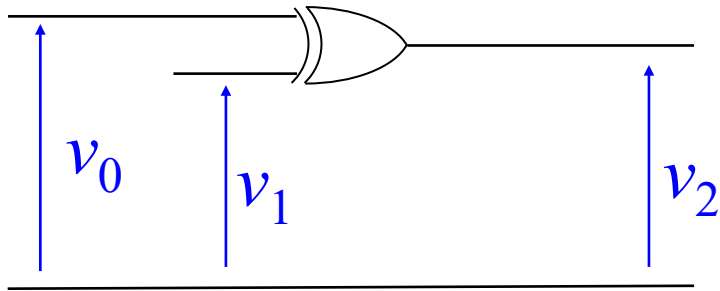

$$Y = \overline{X_1} X_0 + X_1 \overline{X_0}$$

$$= X_1 \oplus X_0$$

v_1 [V]	v_0 [V]	v_2 [V]
0	0	0
0	4.5	4.5
4.5	0	4.5
4.5	4.5	0

真理值表

X_1	X_0	Y
0	0	0
0	1	1
1	0	1
1	1	0


$$Y = \bar{X}_1 X_0 + X_1 \bar{X}_0$$
$$= X_1 \oplus X_0$$

XORのもう一つの論理式


$$\begin{aligned} Y &= \bar{X}_1 X_0 + X_1 \bar{X}_0 \\ &= X_1 \oplus X_0 \end{aligned}$$

XORのもう一つの論理式

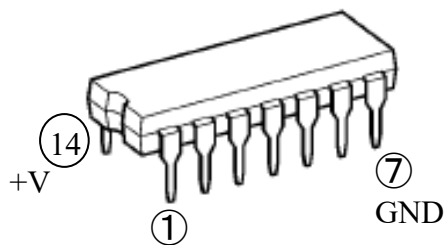
$$\begin{aligned} Y &= \bar{X}_1 X_0 + X_1 \bar{X}_0 \\ &= \overline{\bar{X}_1 X_0 + X_1 \bar{X}_0} \\ &= \overline{(X_1 + \bar{X}_0)(\bar{X}_1 + X_0)} \\ &= \overline{X_1 \bar{X}_1 + X_1 X_0 + \bar{X}_1 \bar{X}_0 + \bar{X}_0 X_0} \\ &= \underline{X_1 X_0 + \bar{X}_1 \bar{X}_0} \end{aligned}$$




デジタルICの立体図

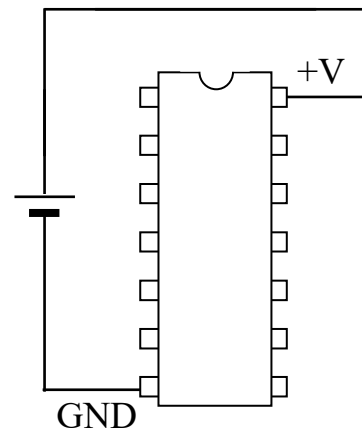


デジタルICの電源配線

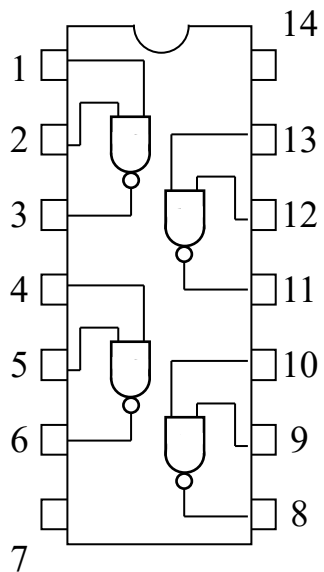

TC74HC00AP
NAND回路

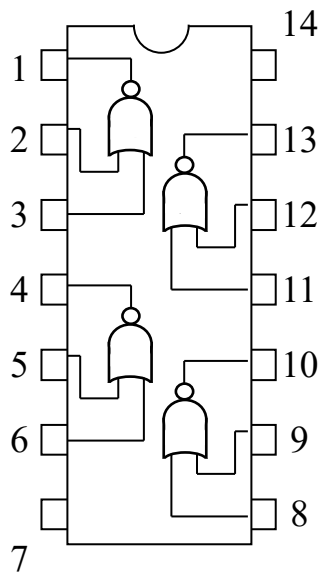

TC74HC02AP
NOR回路

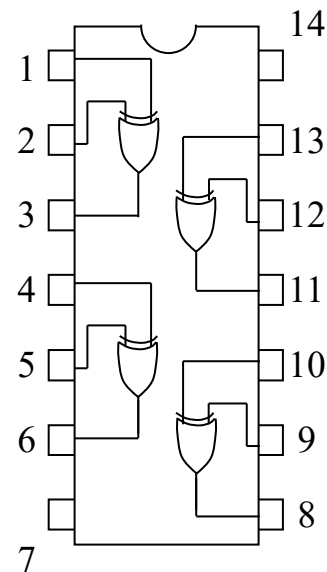

TC74HC86AP
XOR回路

STEP3のレポート課題


NANDによる簡単化

(1)

X_2	X_1	X_0	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$\begin{aligned} \bar{Y} &= \bar{X}_2 X_1 \bar{X}_0 + X_2 X_1 \bar{X}_0 + X_2 X_1 X_0 \\ &= X_1 \bar{X}_0 + X_2 X_1 \\ &= (X_2 + \bar{X}_0) X_1 \end{aligned}$$
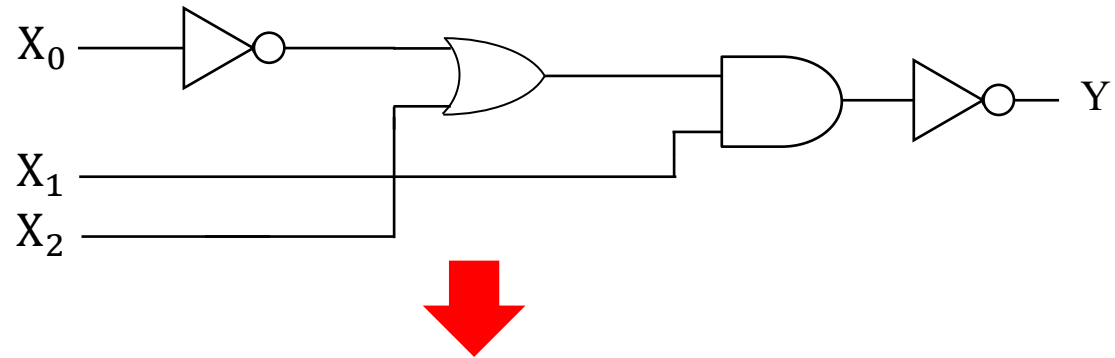
$$\begin{aligned} Y &= \overline{(X_2 + \bar{X}_0) X_1} \\ &= \overline{\overline{\overline{X_2 X_0} X_1}} \end{aligned}$$





STEP3のレポート課題

NANDによる簡単化

(1)

X_2	X_1	X_0	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0
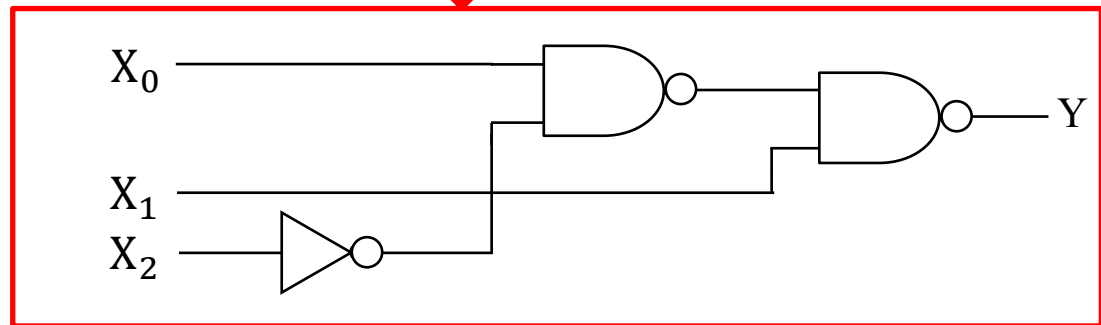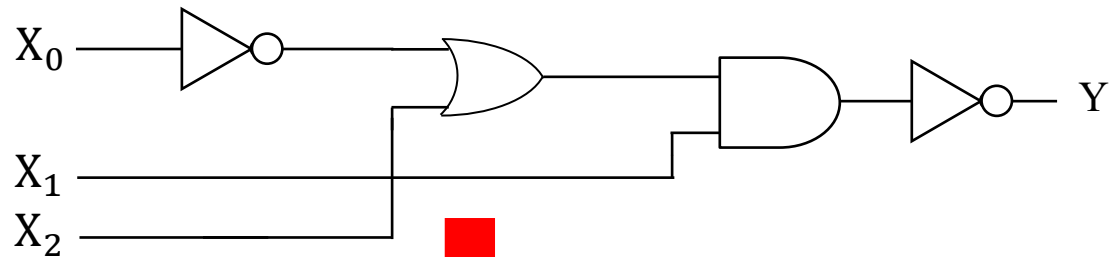
$$\begin{aligned} \bar{Y} &= \bar{X}_2 X_1 \bar{X}_0 + X_2 X_1 \bar{X}_0 + X_2 X_1 X_0 \\ &= X_1 \bar{X}_0 + X_2 X_1 \\ &= (X_2 + \bar{X}_0) X_1 \\ Y &= \overline{(X_2 + \bar{X}_0) X_1} \\ &= \bar{X}_2 X_0 X_1 \end{aligned}$$



STEP3のレポート課題


NAND, NOTによる変形

(2)

X_2	X_1	X_0	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$\begin{aligned} \bar{Y} &= \bar{X}_2 \bar{X}_1 \bar{X}_0 + \bar{X}_2 \bar{X}_1 X_0 + \bar{X}_2 X_1 \bar{X}_0 \\ &= \bar{X}_2 \bar{X}_1 + \bar{X}_2 \bar{X}_0 \\ &= \bar{X}_2 (\bar{X}_1 + \bar{X}_0) \end{aligned}$$
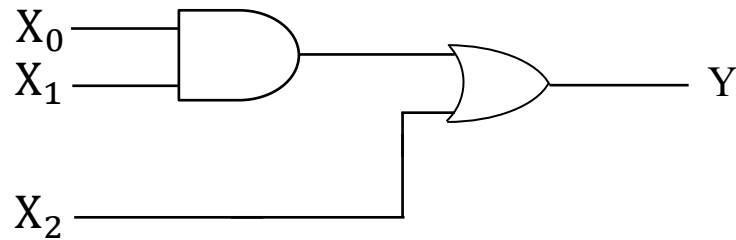
$$\begin{aligned} Y &= \overline{\bar{X}_2 (\bar{X}_1 + \bar{X}_0)} \\ &= \overline{\bar{X}_2} \overline{(\bar{X}_1 + \bar{X}_0)} \\ &= X_2 \bar{X}_1 X_0 \end{aligned}$$





STEP3のレポート課題

NAND, NOTによる変形



(2)

X_2	X_1	X_0	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1
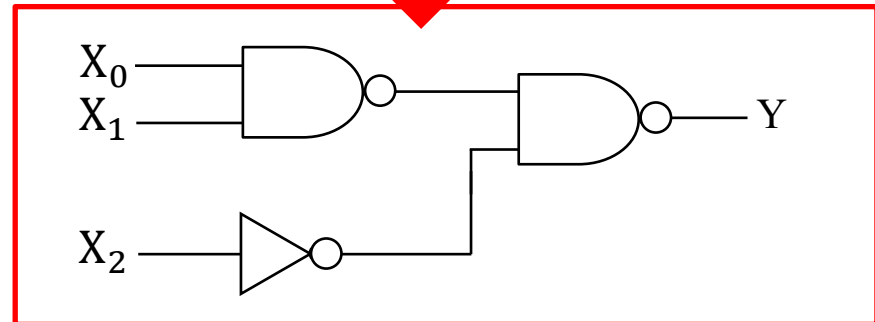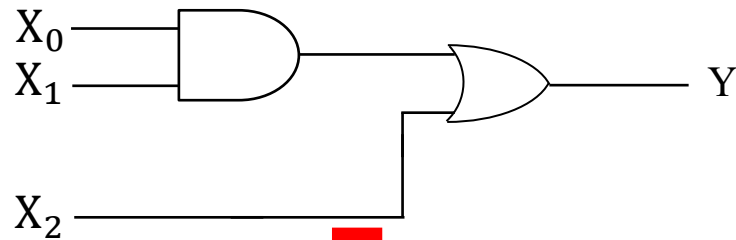
$$\begin{aligned} \bar{Y} &= \bar{X}_2 \bar{X}_1 \bar{X}_0 + \bar{X}_2 \bar{X}_1 X_0 + \bar{X}_2 X_1 \bar{X}_0 \\ &= \bar{X}_2 \bar{X}_1 + \bar{X}_2 \bar{X}_0 \\ &= \bar{X}_2 (\bar{X}_1 + \bar{X}_0) \\ Y &= \overline{\bar{X}_2 (\bar{X}_1 + \bar{X}_0)} \\ &= \overline{\bar{X}_2} \overline{(\bar{X}_1 + \bar{X}_0)} \\ &= X_2 \bar{X}_1 X_0 \end{aligned}$$



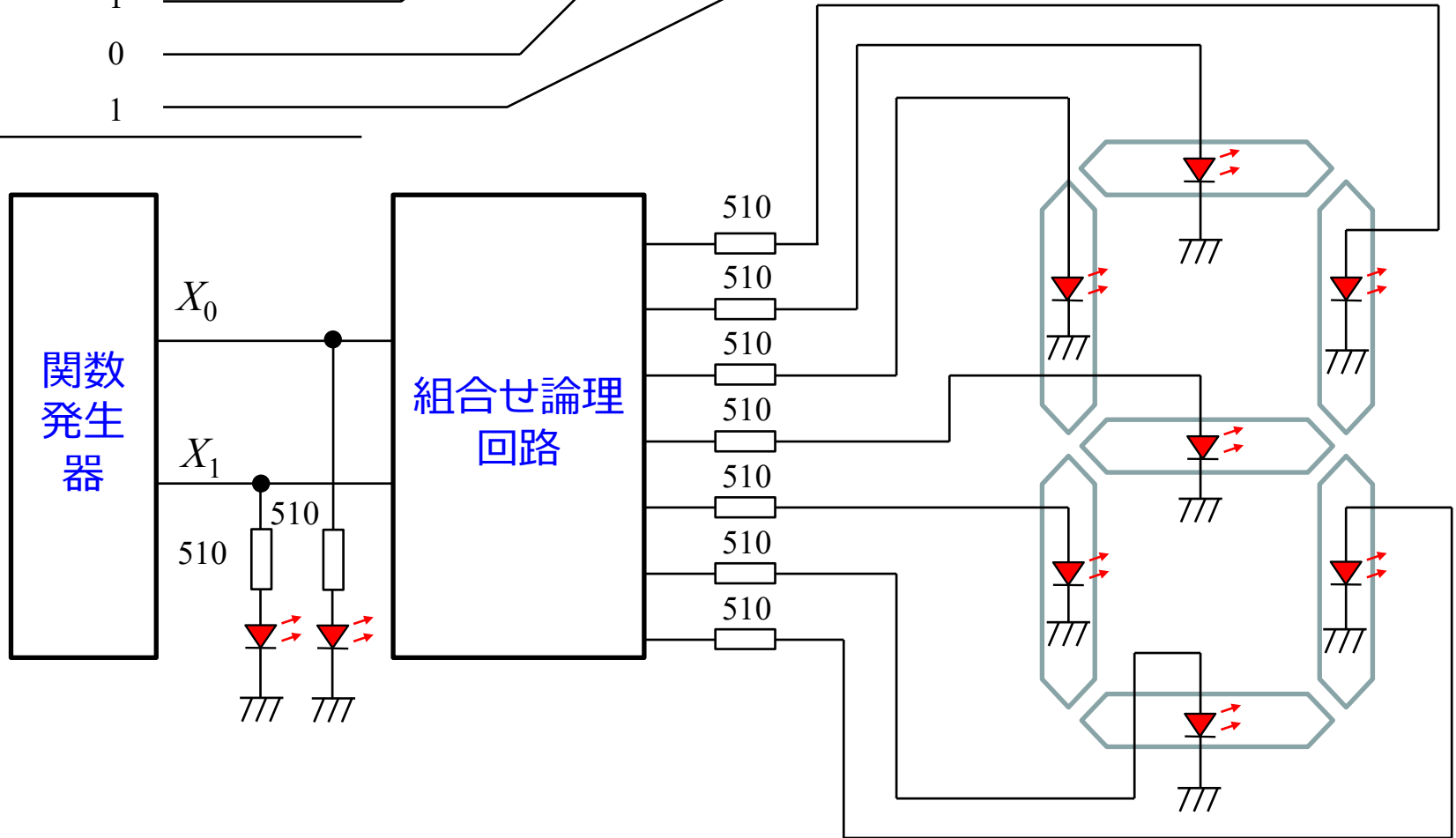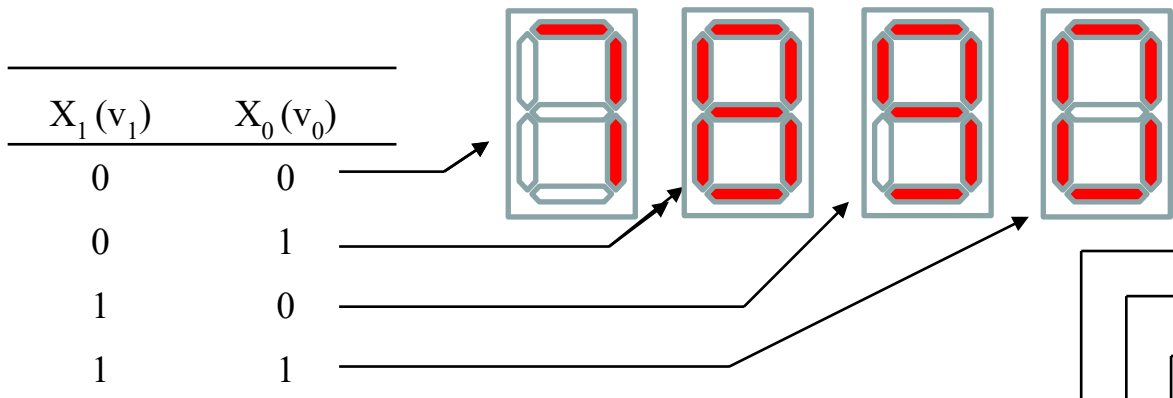STEP5 製作演習 以下の7セグメント表示器の論理回路をNAND, NOR, NOT, XORの中から適当なものを用いて設計せよ。論理回路は3つで済む。導出の過程と、設計した論理回路図も併せて提出せよ。



STEP5 レポート課題 次の真理値表を論理回路で実現せよ。できるだけ論理回路の数を少なくせよ。AND, OR, NOT, NAND, NOR, XORのいずれを用いても良い。導出の過程も示せ。

(ボーナス課題) この論理回路を製作してTAのチェックを受ければ、小問1問につき+1点とする。(締め切り：次回の講義開始時点)

(1)

X_2	X_1	X_0	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

(2)

X_3	X_2	X_1	X_0	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0